

Module 2

Processor organisation

Processor unit:- part of digital computer that implements different operations in the system

Operations:- Arithmetic, logic, shift, transfer

CPU

Combination of processor unit and control unit

All operations are considered as micro operations

Data path:- set of functional units that carry out data processing operation. Data path with a control unit make up the CPU of the computer system


processor unit (data path) + CU \rightarrow CPU

Data paths are controlled using gates.

Methods of organizing processors

- i) bus organization
- ii) shared memory
- iii) Accumulators

i) Bus organisation

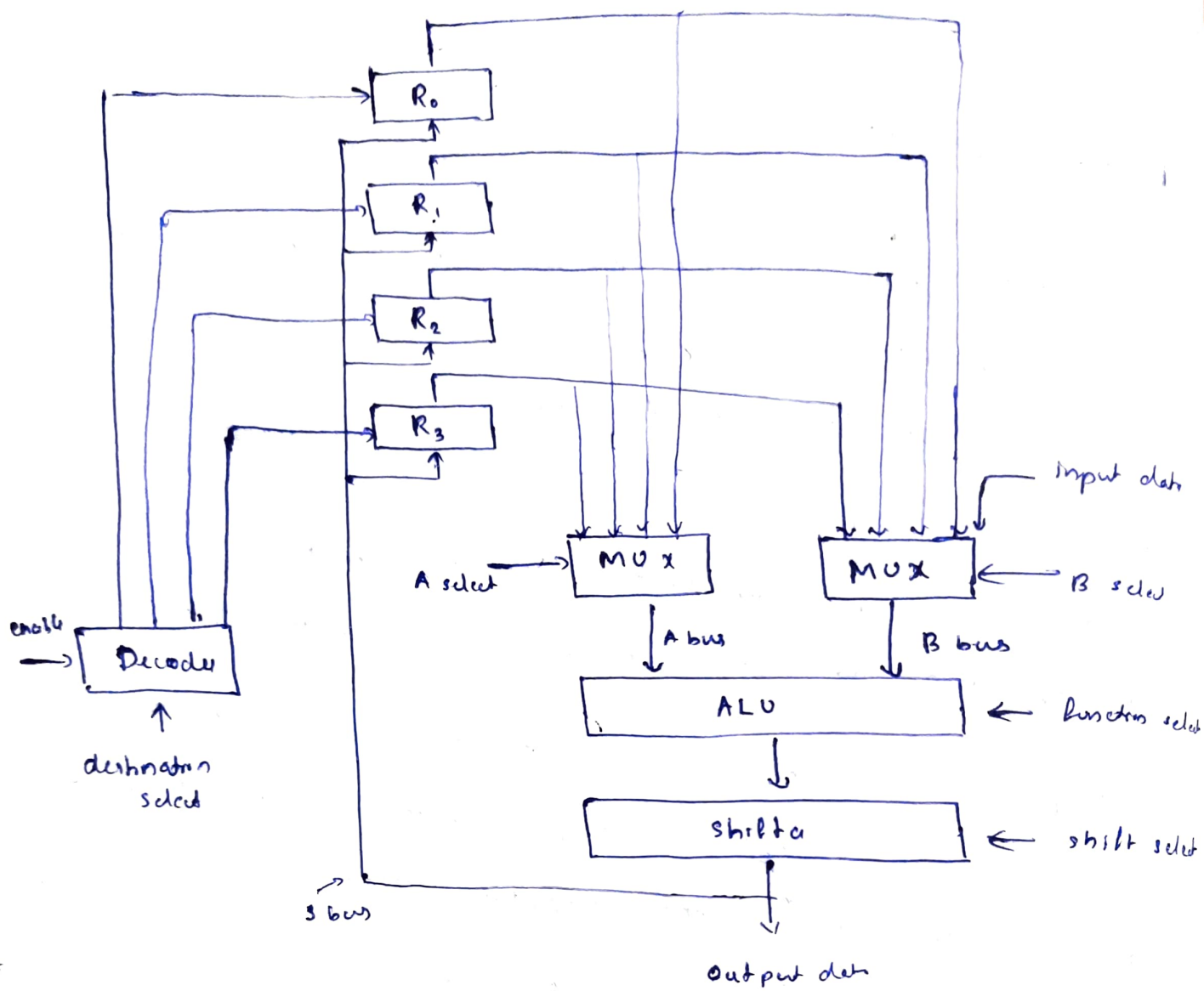

ex. $R_1 \leftarrow R_2 + R_3$

Mux A \rightarrow place the contents of R_2 on Bus A


Mux B \rightarrow R_3 on Bus B

ALU \rightarrow based on fn selection line, it performs $R_2 + R_3$ ($A + B$)

Shifter \rightarrow transfer ALU content to s bus (o/p bus)

decoder \Rightarrow selection R_i and transfer contents of R_i register to R

ii) Scratchpad memory

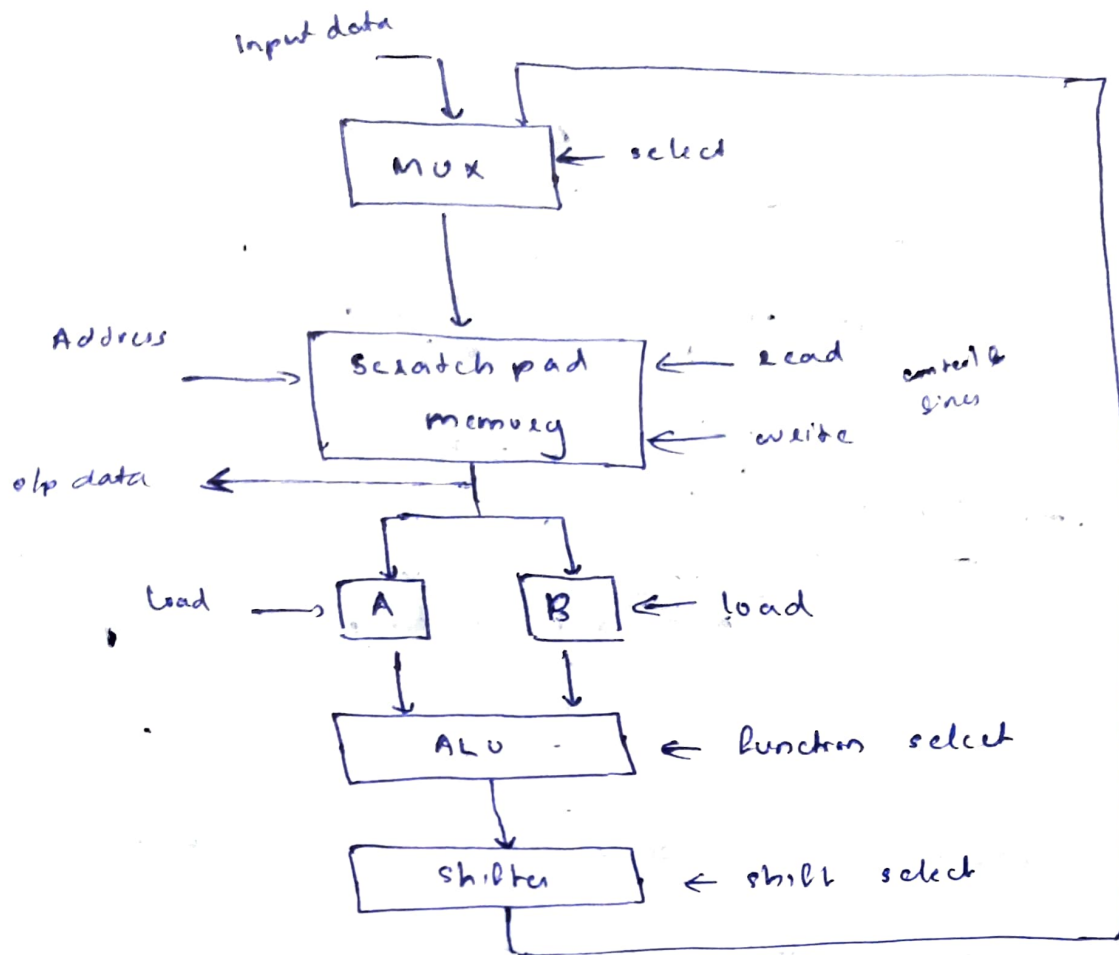

Registers in processor unit can be enclosed within a small memory location unit called scratchpad memory.

A and B are temp registers

- In this memory access operation are more, so it reduces efficiency


$$R_1 \leftarrow R_2 + R_3$$

$T_1 \rightarrow A \leftarrow M[010]$ Read R_2 to bus A

$T_2 \rightarrow B \leftarrow M[011]$ Read R_3 to Bus B

$T_3 \rightarrow M[001]$ store result after performing $A+B$
(Assuming it is destination)

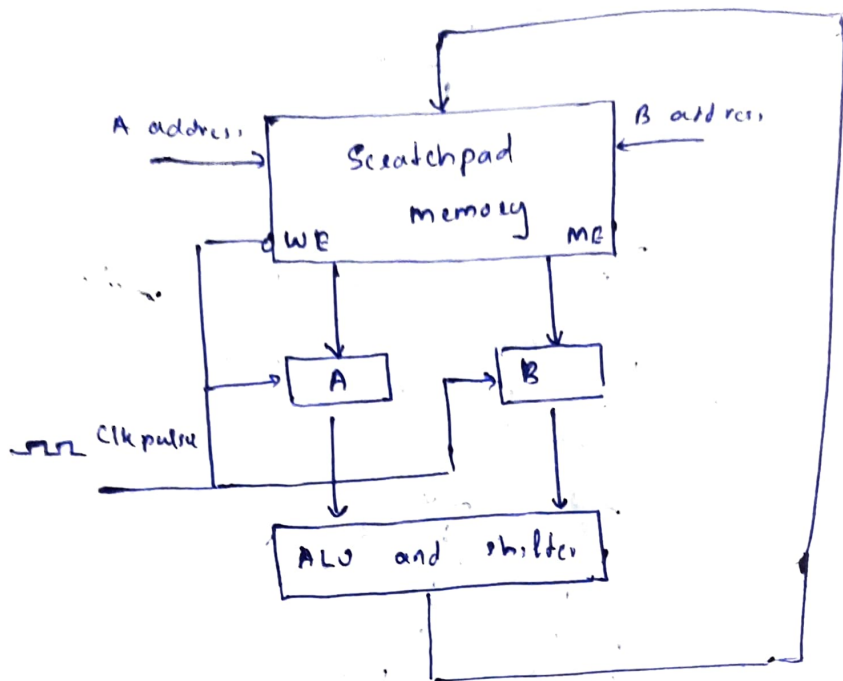46) Solution of this is two port memory (modification of scratch pad)



Here 2 operand address can be read in 1 clk cycle


Using ME (Memory enable) we can choose B as destination register

based on value of clk we can choose Read/Write.

The clock pulse control the memory read and write operation through

the write enable input (WE)

iii) Accumulator

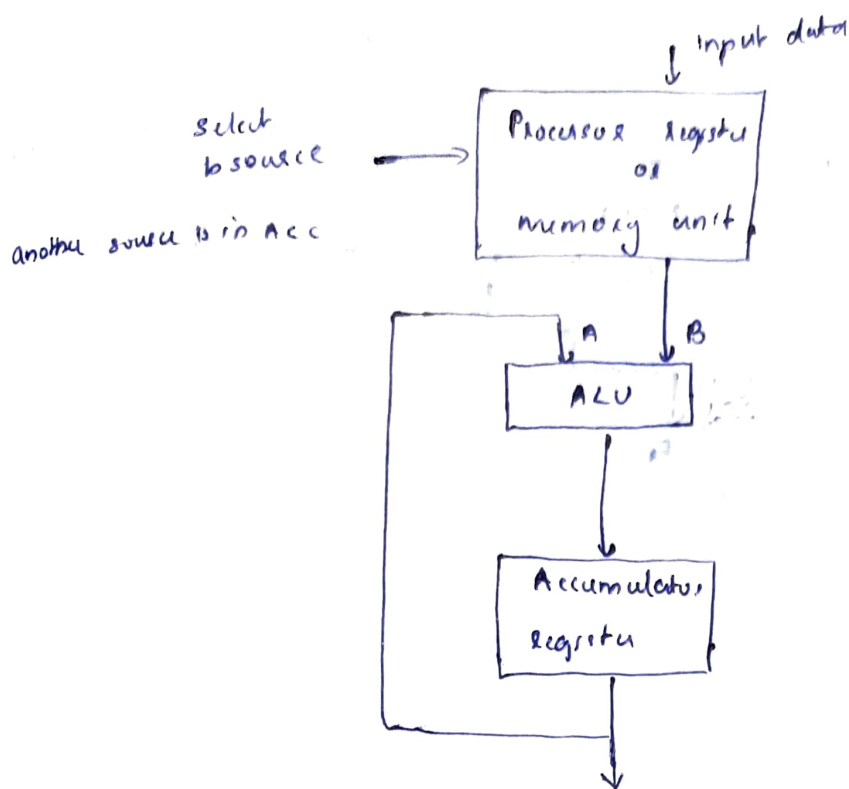

$$R_3 \leftarrow R_1 + R_2$$

T_1 $ACC \leftarrow 0$ clear accumulator

T_2 $ACC \leftarrow ACC + R_1$ transfer contents of R_1 to ACC

T_3 $ACC \leftarrow ACC + R_2$


ALU

It is a digital circuit for performing arithmetic and logic operations.

ALU has a no. of selection lines to select a particular operation. Selection lines are decoded within ALU so that k selection variables can specify upto 2^k operations.

Block diagram of ALU

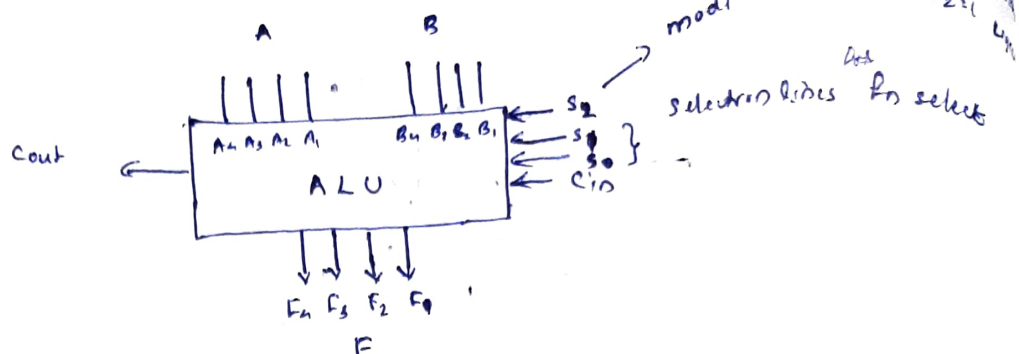we need 2 operands, A and B, which are of 4 bits




Design of arithmetic unit

Arithmetic operations

Addition, subtraction, increment, decrement, arithmetic shift


Parallel adder is used to perform perform these operation.

 To perform n bit addition we require n full adders or $n-1$ full adders and 1 half adder (because initially there is no carry so we can perform addition using half adder)




Using 4 ~~bit~~ ^{Parallel adder} we can perform 8 operation (000 - 111)


1) Addition

 


2) Addition with carry

 


3) A plus 1's complement of B

 


4. subtraction

 


5. Transfer A

 


6. Increment A

 

7. Decrement A

 


8. Transfer A

 

$$6 \rightarrow \begin{array}{r} 0110 + \\ 1111 \\ \hline 10101 \end{array} = 5$$


1st operand is always A, 2nd operand values, 0, 1, B, \bar{B} , so we have to create a circuit which produces these 4 inputs as 1/p to FA

Circuit contains 2 AND, 1 OR and 1 NOT

 


input							output
B	S ₀	S ₁	\bar{B}	BS_0	$\bar{B}S_1$	$BS_0 + \bar{B}S_1$	
0	0	0	1	0	0	0	
0	0	1	1	0	1	1	
0	1	0	1	0	0	0	
0	1	1	1	0	1	1	
1	0	0	0	0	0	0	
1	0	1	0	0	0	0	
1	1	0	0	1	0	1	
1	1	1	0	1	0	1	

S ₀	S ₁	Y
0	0	0
0	1	\bar{B}
1	0	B
1	1	1

 


4 bit arithmetic circuit

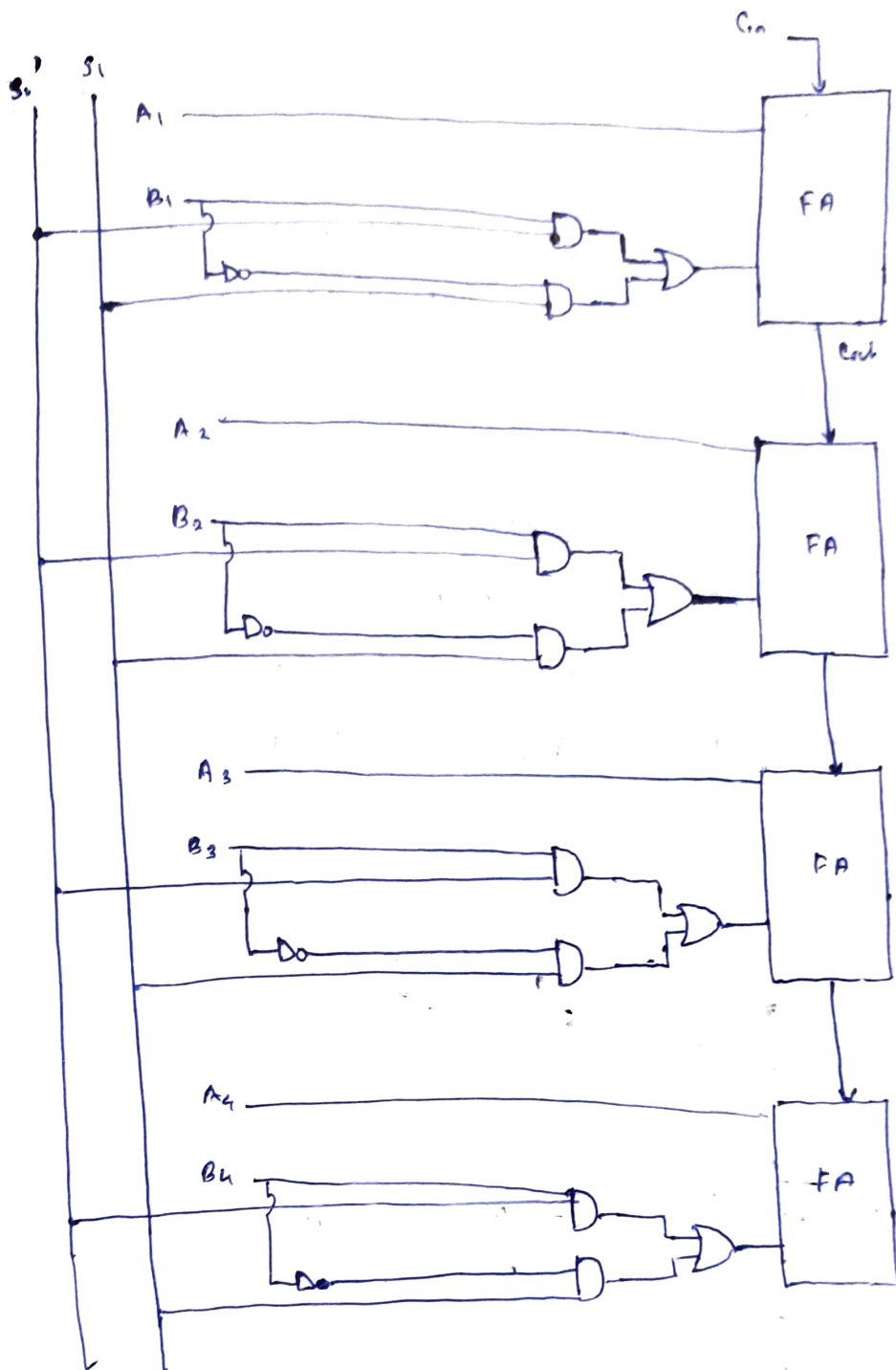

Function table for arithmetic circuit


Selection			Input		Operation	Function
S_1	S_0	C_{in}	A	B		
0	0	0	A	0	Transfer	$F = A$
0	0	1	A	0	Increment	$F = A + 1$
0	1	0	A	B	add	$F = A + B$
0	1	1	A	B	add with carry	$F = A + B + 1$
1	0	0	A	\bar{B}	1's subtraction	$F = A + \bar{B}$
1	0	1	A	\bar{B}	2's subtraction	$F = A + \bar{B} + 1$
1	1	0	A	1	decrement	$F = A - 1$
1	1	1	A	1	Transfer	$F = A$

Design of logic circuit

 


S_1	S_0	Input	function
0	0	$A_i + B_i$	OR
0	1	$A_i \oplus B_i$	XOR
1	0	$A_i \cdot B_i$	AND
1	1	$(A_i)'$	NOT

Complete design of ALU

 

Status register

 Status register is a 4bit register. Four bits are C, Z, S and V. These are set or cleared as a result of an operation performed in the ALU.



For V₀

V is set if no bit greater than 127

Relation	Condition of status bit	Boolean function
$A > B$	$C = 1$ and $Z = 0$	$C \cdot Z'$
$A \geq B$	$C = 1$	C
$A < B$	$C = 0$	C'
$A \leq B$	$C = 0$ or $Z = 1$	$C' + Z$
$A = B$	$Z = 1$	Z
$A \neq B$	$Z = 0$	Z'

Design of shifter

Shifter :

It transfers the output of ALU to the output bus, without a shift with right or left shift.

Shifter can be implemented with bi-directional shift register.

Difficulties in implementation of shifter using bi-directional

- clk pulse is needed for the transfer of information to the shifter.
- ^{another} clk pulse is needed for shift operation.
- another clk pulse is needed for moving information from the shift register to destination registers.


For a single shift operation 3 cycles are required.

5

Implementation of shifter using combinational circuit

The signals from ALU to the output bus propagate through gates without need for a clk pulse. Only one clk pulse is needed in the processor system for loading data from op bus to destination registers.

4 bit combinational logic shifter

 

Function table

H_1	H_0	Operation	Function
0	0	$S \leftarrow F$	Transfer F to S
0	1	$S \leftarrow \text{shr } F$	shift right F into S
1	0	$S \leftarrow \text{shl } F$	shift left F into S
1	1	$S \leftarrow 0$	Transfer 0's into S clear S


right shift

1001 \rightarrow 0100

Processor unit


- selection variables in a processor unit control, the micro-operation executed within processor during any clk pulse
- selection variable controls
 - buses
 - ALU
 - shifter
 - destination register

Block diagram

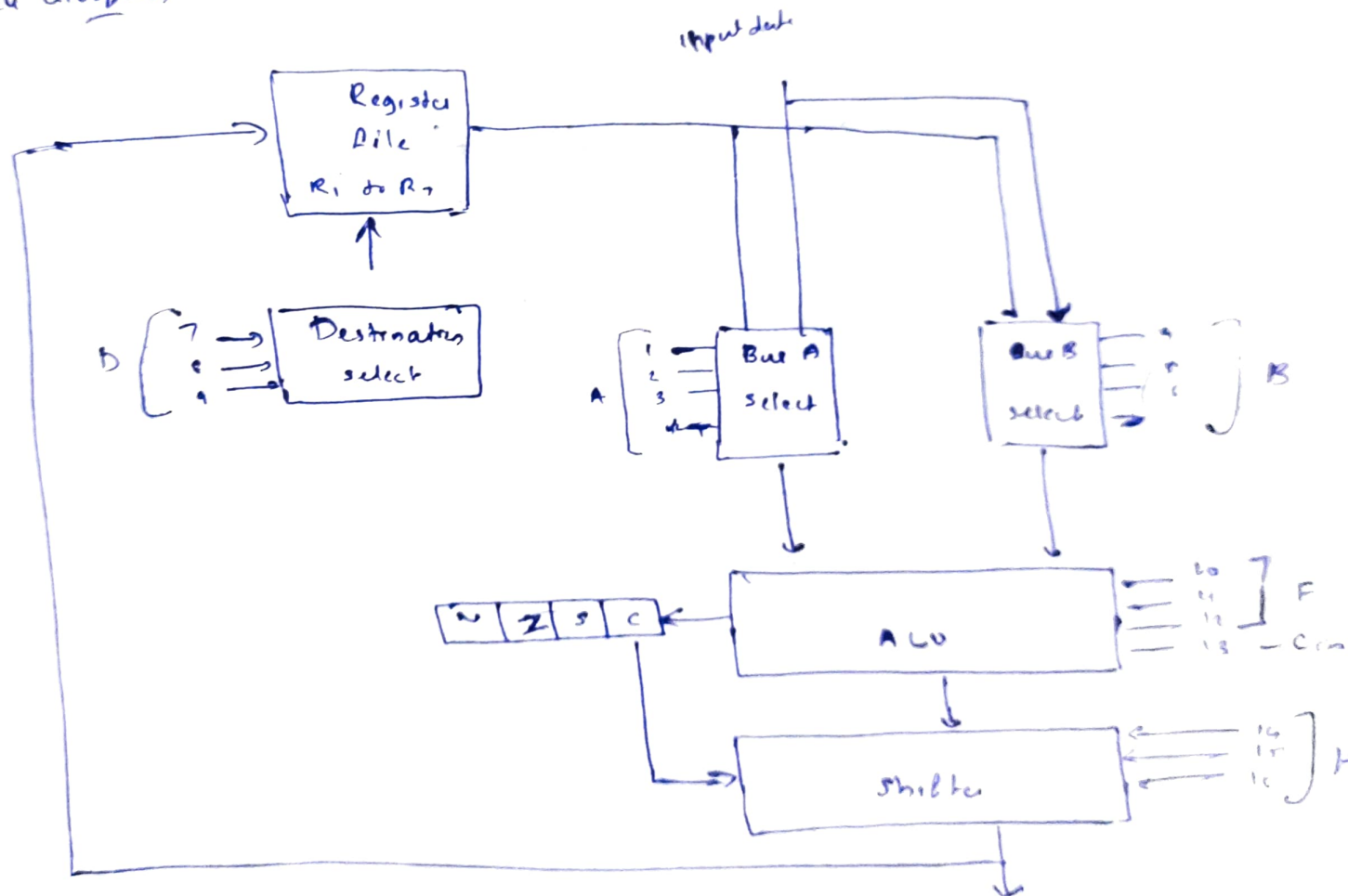

another selection line for circular shift

 - It consists of 7 registers R_1 ~~to~~ R_7 and a status register.
- The v/p go through 2 multiplexers to select the ip to ALU.
- If data from an external source are also selected by the same multiplexers. The output of ALU goes through a shifter and transferred to any one of the registers.
- In this there are 16 selection variables for the unit and P_n is specified in control word.



- 3 bits A \rightarrow select a source register for the input ~~to the left~~ side of ALU.
- 3 bits of B \rightarrow select a source register for the input to the right side of ALU.
- 3 bits of D \rightarrow select destination register.
- 3 bits of F + 1 bit of C_{in} \rightarrow select function for ALU.
- 3 bits of H \rightarrow select the type of shift in the shifter unit.

Function of selection variables

Binary code	A	B	D	F with $C_{in} = 0$	F with $C_{in} = 1$	H
0 0 0	Input data	Input data	None	$A, C_{in} = 0$	$A+1$	No shift
0 0 1	R_1	R_1	R_1	$A+B$	$A+B+1$	shift right, $C_{in} = 0$
0 1 0	R_2	R_2	R_2	$A-B-1$	$A-B$	shift left, $C_{in} = 0$
0 1 1	R_3	R_3	R_3	$A+1$	$A, C_{in} = 1$	0's in op bus
1 0 0	R_4	R_4	R_4	$A \vee B$	-	-
1 0 1	R_5	R_5	R_5	$A \oplus B$	-	Calculate right with C
1 1 0	R_6	R_6	R_6	$A \wedge B$	-	Calculate left with C
1 1 1	R_7	R_7	R_7	\bar{A}	-	-

1) $A=B=000$ then mux selects input data (not value from registers) and no destination is selected, $D=000$

2) 2 bits in F added together with 1st carry from previous micro operation of ALU

3) 1st 4 entries of op code in H field specify the shift operation of logic shifter.

$$R_1 \leftarrow R_1 - R_2$$

Find the control word

an

001	010	001	010	1	000
-----	-----	-----	-----	---	-----

A B D E Cn H

R_1 - left ip of ALU

R_2 - right ip of ALU


A-B is ALU operation

no shift required

R_1 destination register

Design of accumulator

Block diagram

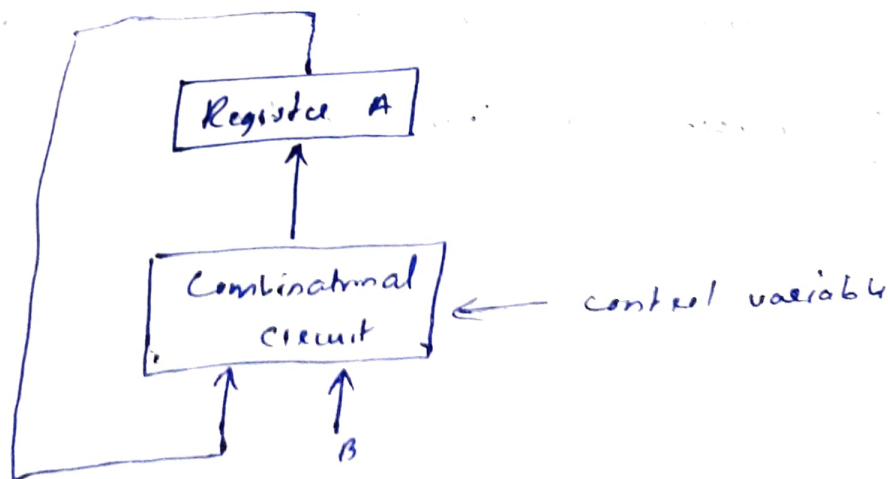

Data inputs

The external inputs to accumulator are the data input from B and the control-variable, that determine the micro operation. For the register. The next state of register A is a function of the present state of and the external inputs.

Accumulator can also perform data processing operations. Total of nine operations is considered here for the design of accumulator circuit.

Control variable	Microoperation	Name
P_1	$A \leftarrow A + B$	Add
P_2	$A \leftarrow 0$	clear
P_3	$A \leftarrow \bar{A}$	complement
P_4	$A \leftarrow A \wedge B$	AND
P_5	$A \leftarrow A \vee B$	OR
P_6	$A \leftarrow A \oplus B$	EX-OR
P_7	$A \leftarrow \text{shr } A$	shift right
P_8	$A \leftarrow \text{shl } A$	left shift
P_9	$A \leftarrow A + 1$	increment
	$\text{if } (A=0), \text{ then } (Z=1)$	check for zero

A bit accumulator

